



Announcements

- Homework
 - Video Homework due tonight
 - Webwork 15 due on Wednesday
 - Nothing due Friday. Study up!
 - Also nothing due the Monday after Spring break. Relax!
- Test 2 on Friday!
 - You get a new notecard
 - Study materials are posted
 - Same general style as Test 1
 - Will probably be on an honor system, where I will send it out and you have like 1.25 hours to complete, photograph, and email it back to me.
- Tutoring is still happening. See Campuswire for info!
- Need to ask questions or talk with me personally? Email me and we can set up a time to meet in person or via Zoom.
- Polling: `rembold-class.ddns.net`



Capacitor Addition

In Parallel

- Each plate of the capacitor connected to other capacitor plates
- As if all the plates were touching, forming one large plate
- Since capacitance is proportional to A , we can get the total capacitance by adding

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

In Series

- Negative plates connected to positive plates
- Neutral \Rightarrow same charge on each
- Conservation of energy thus says

$$\mathcal{E} - \frac{Q}{C_1} - \frac{Q}{C_2} - \frac{Q}{C_3} = 0$$


- Same as

$$\mathcal{E} - Q \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)}_{1/C_{eq}} = 0$$



Capacitor Circuits

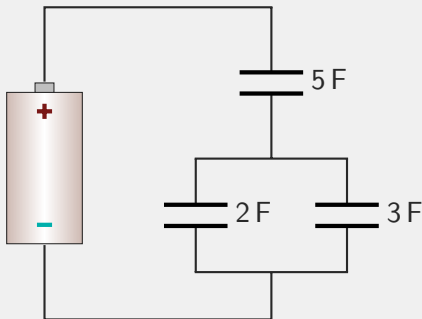What is the equivalent capacitance of the circuit shown to the right?



Solution: 2.5 F




Understanding Check

Given the circuit to the right, what amount of charge is on the middle capacitor when the circuit reaches steady state? You are told that

$$\mathcal{E} = 5\text{ V} \quad C_1 = 2\text{ F}$$

$$C_2 = 4\text{ F} \quad C_3 = 2\text{ F}$$

- A) 8 C
- B) 4 C
- C) 2 C
- D) 0.8 C

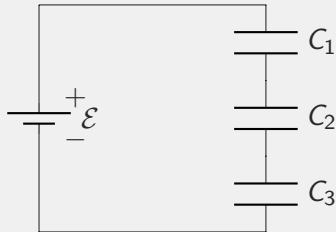

Solution: 4 C



Energy Considerations

- Would like to be able to talk about the energy stored in a capacitor in term of its capacitance
- Recall that

$$\Delta U = \frac{1}{2} \epsilon_0 E^2 (\text{volume})$$

- We can thus write:

$$\begin{aligned} \Delta U &= \frac{1}{2} \epsilon_0 \left(\frac{Q}{A \epsilon_0} \right)^2 (As) = \frac{1}{2} \epsilon_0 \frac{Q^2}{A^2 \epsilon_0^2} (As) \\ &= \frac{1}{2} \frac{Q^2 s}{\epsilon_0 A} = \frac{1}{2} \frac{(C \Delta V)^2}{C} \\ &= \frac{1}{2} C (\Delta V)^2 \end{aligned}$$



So, about those dielectrics now...

- Recall that, with the dielectric inserted, the electric field inside the capacitor is

$$E_{insulator} = \frac{E_{w/o}}{K}$$

- Then the potential difference is

$$\Delta V = E_{insulator}s = \frac{E_{w/o}s}{K} = \frac{\Delta V_{w/o}}{K}$$

- So the capacitance is

$$C = \frac{Q}{\Delta V} = \frac{Q}{\frac{\Delta V_{w/o}}{K}} = KC_{w/o}$$

- So inserting a dielectric *increases* the capacitance of our capacitor!



Glass Example

Suppose we have a capacitor with a capacitance of $100\ \mu\text{F}$ with a vacuum between the charged plates. We charge it to $10\ \text{V}$ and then insert a piece of glass with a dielectric constant of 8 between the plates. How much additional charge can be placed on the capacitor plates? How much more energy can the capacitor store now?

Solution: $7\ \text{mC}$, $35\ \text{mJ}$



Resistance

- We've already been talking about resistance
 - In terms of:
 - electron density
 - electron mobility
 - cross-sectional area
- This is great when taking a microscopic view, but not as useful for an everyday, macroscopic perspective
- Want to start eliminating or separating out the various dependencies

Current Density

We define the current density J to be

$$J = \frac{I}{A}$$

with units of A/m^2 .



Conductance

- In our current equation:

$$I = |q|nAuE$$

q , n and u are all basically properties of the metal

- Would be useful to wrap them all up together so we just have one lump “property” to consider
- Just realize this technically hides information from us!

Conductance

We define the conductivity (σ) of a metal to be

$$\sigma = |q|nu$$

with units of A/V, also called Siemens (S)



A Macroscopic Take

- All told, we now can write:

$$J = \frac{I}{A} = \sigma E$$

- Over a certain length of wire, we also know that:

$$|\Delta V| = EL$$

- Combining terms:

$$\begin{aligned} \frac{I}{A} &= \sigma \left(\frac{\Delta V}{L} \right) \\ I \left(\frac{L}{\sigma A} \right) &= \Delta V \end{aligned}$$



Resistance

We define the constants in parentheses to be the resistance:

$$R = \frac{L}{\sigma A}$$

where R has units of ohms (Ω) or V/A

- Contains all the electronic and geometric properties of the wire/resistor all wrapped up in a nice single parameter
- Easy to relate the current to the potential difference:

$$\Delta V = IR$$



Wire Resistance

We looked at several problems where we were using short copper wires. What is the resistance of a 30 cm long, 1 mm diameter copper wire? We know that, for copper, $n = 8.5 \times 10^{28} \text{ e}^-/\text{m}^3$ and $u = 4.4 \times 10^{-3} \text{ (m/s)/(N/C)}$.

Solution: 6.38 m Ω



Going Zen: Ohhhmmmmm...

- Resistance is only useful to us as a mostly fixed parameter
 - Means n and u shouldn't change much depending on current
- Materials where n and u are mostly constant with current are called **ohmic**.
- By comparison, **non-ohmic** materials have their electric properties change significantly depending on current (and temperature)
- Most metals are only roughly ohmic, so long as the currents are low
- Semiconductors: seriously non-ohmic
 - n varies greatly on voltage
 - Low voltage means n is incredibly small, \Rightarrow basically zero current
 - Double the voltage and n and get huge, \Rightarrow lots of current!
 - Let's you turn on/off segments of wire depending on voltage