



Announcements

- Homework
 - Webwork 15 is due tonight
 - Will be an Webwork due Friday, but not over break
- Test 2 is postponed
 - Chapters 16 – 19
 - Probably have it Wednesday or Friday after break
- Polling: `rembold-class.ddns.net`



Adding Resistors

In Series

- By loop law:

$$\mathcal{E} - R_1 I - R_2 I - R_3 I = 0$$

- Current same through series

$$\mathcal{E} - \underbrace{(R_1 + R_2 + R_3)}_{R_{eq}} I = 0$$

- So in series:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

In parallel

- Same loop law
- \mathcal{E} the same in parallel

$$I - \mathcal{E} \underbrace{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}_{1/R_{eq}} = 0$$


- So in parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



Simplifying Circuits

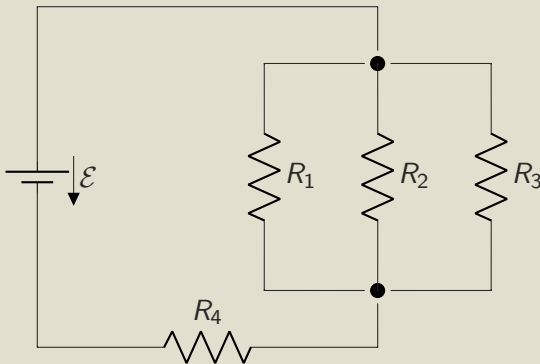Reduce the below circuit to a single resistor and determine its equivalent resistance.



$$R_1 = 50 \, \Omega$$

$$R_2 = 75 \, \Omega$$

$$R_3 = 100 \, \Omega$$

$$R_4 = 25 \, \Omega$$


Solution: $48.1 \, \Omega$



Understanding Check!

Given the circuit to the right, what is the equivalent resistance?

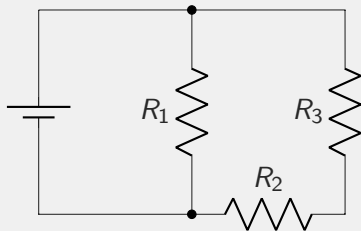- A. $5\ \Omega$
- B. $8.86\ \Omega$
- C. $12\ \Omega$
- D. $20\ \Omega$



$$R_1 = 10\ \Omega$$

$$R_2 = 6\ \Omega$$

$$R_3 = 4\ \Omega$$

Solution: $5\ \Omega$



Ultimate Power in the Universe...

- Lightbulbs (or any resistor) don't use up current
 - But they do transform energy to light and heat
 - Rate at which they do so determines brightness
- Mathematically:

$$\text{Power} = \frac{\Delta U}{\Delta t} = \frac{\Delta q \Delta V}{\Delta t} = I \Delta V$$

- Can also be related to the resistance:

$$\text{Power} = I \Delta V = I^2 R = \frac{(\Delta V)^2}{R}$$

- Energy dissipated through a circuit component will depend on both the current and the potential difference across that circuit element



Lightbulb!

Suppose you have three equivalent lightbulbs. How can you hook them up to a battery to ensure the greatest possible output of total light?

Solution: All in parallel



Back to Batteries


- Have been assuming perfect batteries
 - only force felt would be from the conveyor belt
 - What about the electrostatic forces from charges already moved?
- Would give opposing force:

$$\vec{F}_{net} = \vec{F}_{batt} - e\vec{E}_{batt}$$

- Finding the change in potential:

$$\Delta V = (F_{batt} - eE_{batt}) \frac{s}{e}$$
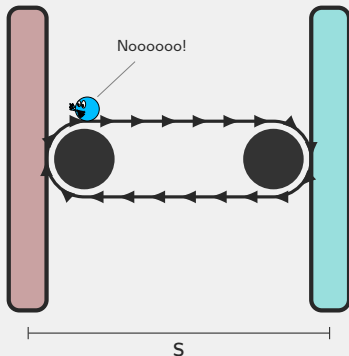
$$\Delta V = \mathcal{E} - E_{batt}s = \mathcal{E} - r_{int}I$$





Ideal Battery

Suppose you have a 9 V battery which, when hooked up to a $100\ \Omega$ resistor only creates a current of only 75 mA . What is the internal resistance of the battery?

Solution: $20\ \Omega$



When does it matter?

Take the same battery and compare its ideal and real currents for a selection of resistances:

Circuit Resistor	Ideal ($r_{int} = 0$)	Real ($r_{int} = 20\ \Omega$)
100 Ω	90 mA	75 mA
1000 Ω	9 mA	8.8 mA
10 k Ω	0.9 mA	0.898 A



When does it matter?

Take the same battery and compare its ideal and real currents for a selection of resistances:

Circuit Resistor	Ideal ($r_{int} = 0$)	Real ($r_{int} = 20\ \Omega$)
10 Ω	0.9 A	0.3 A
100 Ω	90 mA	75 mA
1000 Ω	9 mA	8.8 mA
10 k Ω	0.9 mA	0.898 A

Internal resistance can make a huge difference when the resistances are small!